

**Class Note 07:  $\Delta \leftrightarrow Y$  Transformation Example**

**Problem Setting:**

Find currents  $i_0$ ,  $i_1$ , and  $i_2$  of the circuit below.

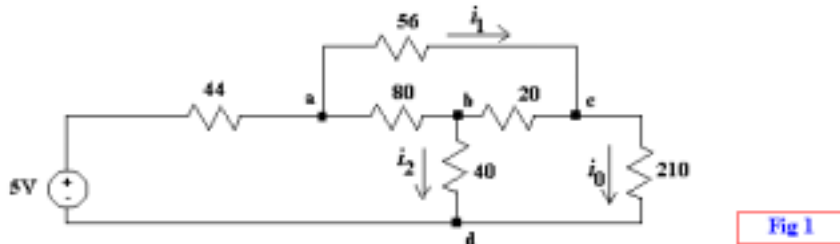


Fig 1

**SOLUTION**

1. Let's observe the circuit before we make any move. Do you see Y and  $\Delta$  resistors?

Yes, we see them as shown below. But remember, in most of circuit problems, it's an one way traffic as far as the transformation direction concerns:  $\Delta \rightarrow Y$ .

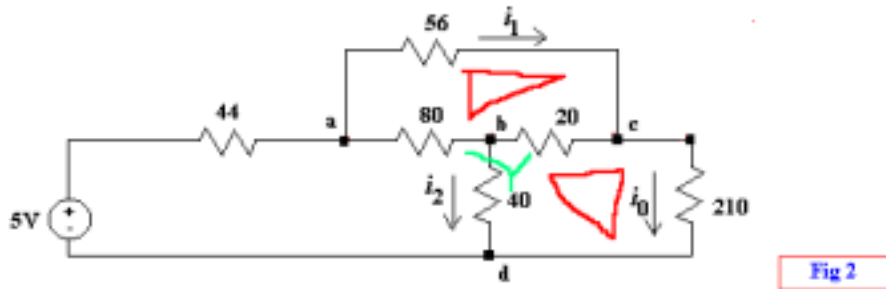


Fig 2

2. If you convert the  $\Delta$  resistors (right side) to Y then it looks like this: *Why not the top  $\Delta$ ?*

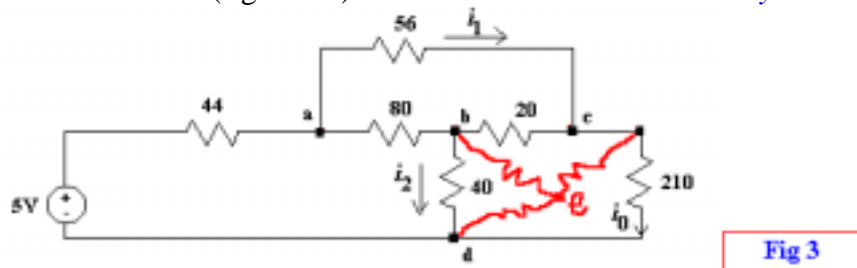


Fig 3

Here we have to remember that:  $i_2 = \frac{V_{bd}}{40}$  and  $i_0 = \frac{V_{cd}}{210}$ ;  $i_1$  is the current through  $56\Omega$  resistor

3. Now we have the following simplified circuit:

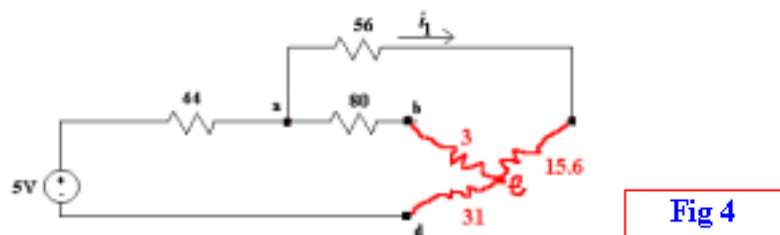


Fig 4

4. It further simplifies to:

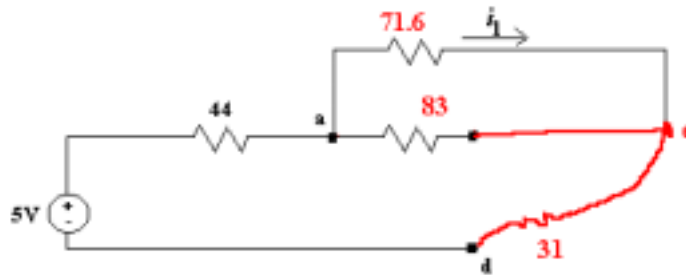


Fig 5

4. Finally, the circuit is reduced to a single loop one:

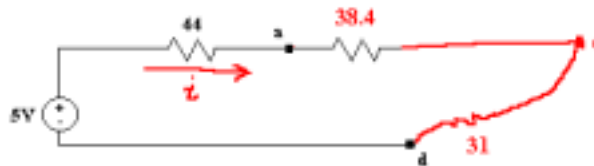


Fig 6

5. Then the current flowing through the resistors is:  $i = \frac{5}{(44 + 38.4 + 31)} = 0.044 \text{ [A]}$  (Fig.6)

6. Now let's find currents by the following steps: (it looks like a wave propagation, or, stating from an open cell, marking mines or opening neighboring cells, in your famous minesweeper game. Or do you feel it?)

(1) The voltage  $V_{ae} = 0.044 \times 38.4 = 1.69 \text{ [V]}$  (Fig.6)

(2) Therefore the current  $i_1 = \frac{V_{ae}}{71.6} = 0.0236 \text{ [A]}$  (Fig.5)

(3) The current through the 80 resistor is:  $i_{80} = \frac{V_{ae}}{83} = 0.02036 \text{ [A]}$  (Fig. 4)

(4) Therefore, voltage  $V_{ab} = i_{80} \times 80 = 1.63 \text{ [V]}$  (Fig.4 and Fig.3)

(5) Also, voltage  $V_{ad} = i \times (38.4 + 31) = (0.044)(69.4) = 3.0536 \text{ [V]}$  (Fig. 6)

(6) Then, from above two voltages, we have voltage:

$$V_{bd} = V_{ad} - V_{ab} = 3.0536 - 1.63 = 1.4236 \text{ [V]} \text{ (Fig. 3)}$$

(7) Then, current  $i_2 = \frac{V_{bd}}{40} = \frac{1.4236}{40} = 0.0356 \text{ [A]}$  (Fig. 3)

(8) By KCL at node  $b$ , we get the current through 20 resistor (toward right):

$$i_{20} = i_{80} - i_2 = -0.01524 \text{ [A]} \text{ (Fig. 2)}$$

(9) Therefore,  $i_0 = i_1 + i_{20} = 0.0236 + (-0.01524) = 0.00836 \text{ [A]}$  (Fig. 2)